
# DLD LAB 06:


# Q4:

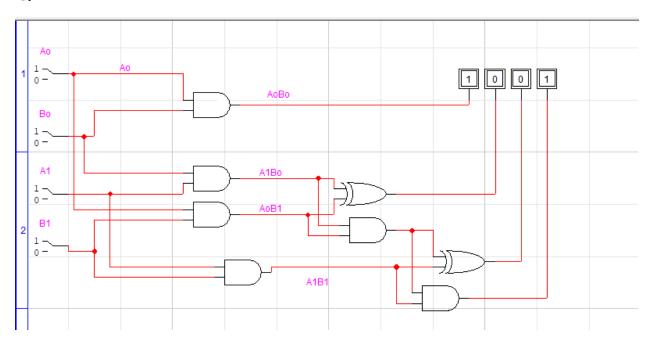

# TruthTable:

A1	Ao	B1	Во	A1Bo	AoB1	A1B1	AoB1+A1Bo	С	A1B1+C	AoBo
0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0
0	1	0	1	0	0	0	0	0	0	1
0	1	1	0	0	1	0	1	0	0	0
0	1	1	1	0	1	0	1	0	0	1
1	0	0	0	0	0	0	0	0	0	0
1	0	0	1	1	0	0	1	0	0	0
1	0	1	0	0	0	1	0	0	1	0
1	0	1	1	1	0	1	1	0	1	0
1	1	0	0	0	0	0	0	0	0	0
1	1	0	1	1	0	0	1	0	0	1
1	1	1	0	0	1	1	1	0	1	0
1	1	1	1	1	1	1	1	1	1	1

# Q5:

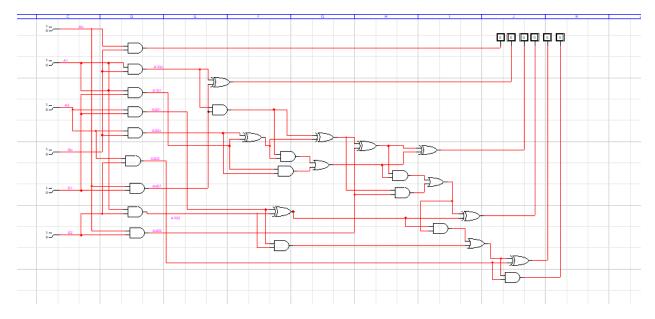

## Q6:

# 4-bit Adder:

